

### Question block created by wizard

This exam contains 40 questions.

1. What type of diode is shown here?



- a. This is the symbol of a zener diode.
- b. This is the symbol of a tunnel diode.
- c. This is the symbol of a shottky diode.


2. What is in excess present in P type semi-conductor material?

- a. Holes
- b. Non.
- c. Electrons.

3. Which of the following answers gives a typical value of forward current for a small-signal silicon diode?

- a. 10 mA
- b. 1 A
- c. 10 A

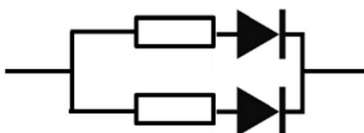4. See figure. What is the purpose of the resistor in series with each diode?




- a. To assure that each diode has the same voltage applied.
- b. To increase the breakdown voltage across each diode.
- c. To equal out the difference in the diodes.

5. What is the name of the control connection of a thyristor?

- a. Gate.
- b. Anode.
- c. Cathode.

6. What is a typical characteristic of a Varistor?
- The output voltage decreases when the input voltage increases.
  - When the voltage exceeds a certain level, its resistance will drop.
  - With the increasing of voltage the variable resistor value will increase.

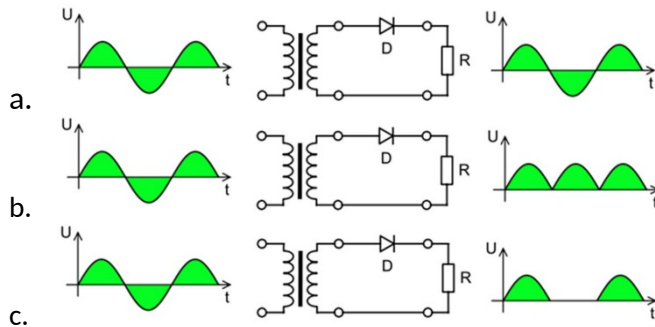7. What is the correct picture for the voltage across the load resistor?



8. A diode, measured both ways with an ohm meter, indicates infinite one way and zero the other way. What is your conclusion about this diode?

- The diode is shorted and defective.
- The diode is good.
- The diode is open and defective.

9. The region inside a diode where no free charge carriers exist is known as the:

- conduction layer
- depletion layer
- insulation layer


10. The stripe on a plastic encapsulated diode usually indicates the:

- anode connection.
- cathode connection.
- earth or ground connection.

11. An atom with 5 electrons in its outer shell is part of

- a C type material
- a P type material
- a N type material

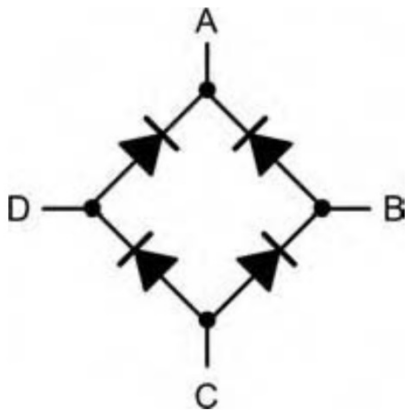- 12.** A silicon diode, when compared to a germanium diode has
- the same forward bias voltage
  - a higher forward bias voltage
  - less forward bias voltage
- 13.** To check the forward resistance of a diode with a multi-meter, the lead connected to the positive terminal is put to the
- cathode
  - anode
  - either anode or cathode
- 14.** A germanium diode has an upper temperature limit of about...
- 80° - 100°C
  - 150° - 200°C
  - 250° - 300°C
- 15.** At which terminals the alternating current input should be connected to the bridge rectifier shown?



- B and D
- A and B
- A and C

16. This symbol is



- a. a laser diode
- b. a photodiode
- c. an LED

17. A typical application for a Zener diode is:

- a. controlling the current in a load.
- b. acting as a variable capacitance in a tuned circuit.
- c. regulating a voltage supply.

18. The device shown in the figure is:



- a. a junction gate field effect transistor.
- b. an NPN bipolar junction transistor.
- c. a PNP bipolar junction transistor.

19. In an NPN transistor the P type material is the?

- a. emitter
- b. collector
- c. base

20. In normal operation of a bipolar NPN junction transistor....

- a. the base-emitter junction is reverse biased and the collector-base junction is forward biased.
- b. both junctions are forward biased.
- c. the base-emitter junction is forward biased and the collector-base junction is reverse biased.

21. What are the two junctions of a transistor?

- a. emitter-base and collector-emitter

- b. Emitter-base and emitter-collector
- c. emitter-base and base-collector

**22.** Which way does conventional current flow in a PNP junction?

- a. Emitter to base.
- b. Collector to emitter.
- c. Collector to base.

**23.** The connections to a JFET are labelled:

- a. collector, base and emitter.
- b. anode, cathode and gate.
- c. source, gate and drain.

**24.** A FET when compared to a junction transistor is

- a. high impedance.
- b. low impedance.
- c. current operated.

**25.** The common collector amplifier is sometimes called the emitter follower circuit because


- a. the emitter current follows the collector current.
- b. the emitter voltage follows the base voltage.
- c. the emitter voltage follows the collector voltage.

**26.** Which class of amplifier allows collector current to flow for a full 360 degrees of the input signal?

- a. Class A
- b. Class B
- c. Class C

27. In the figure you see a push-pull amplifier. The transistor TR2 and TR3 are from different types. One is a PNP transistor and the other a NPN transistor.

Why are used two different transistors?

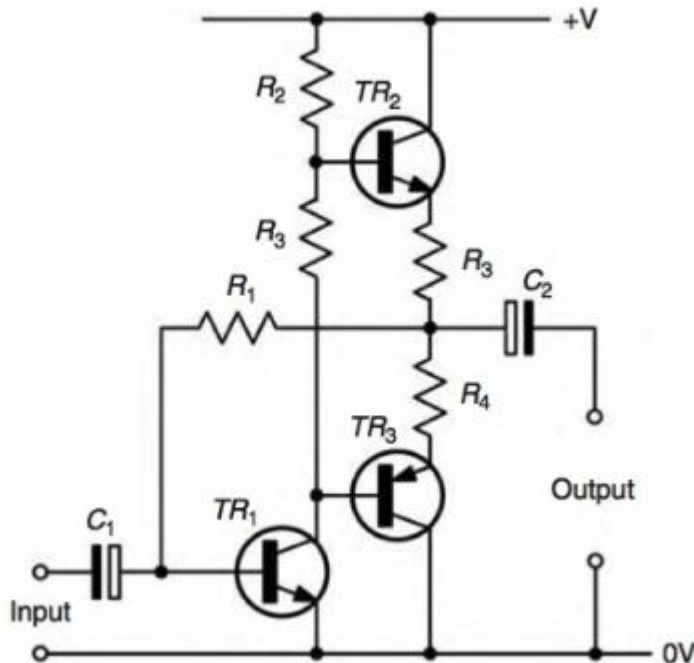


- Both transistors work together at the same time to produce more power at the output.
  - It is not necessary to use two different transistors. It is also possible to use the same type of transistor.
  - One transistor amplifies the positive half and the other transistor amplifies the negative half of the input signal.
28. The function of a NOT logic gate within a circuit is to....
- ensure the output signal is of the same state as the input signal.
  - invert the input signal so that the output is always of the opposite state.
  - ensure the input signal is DC only.
29. The following symbol represents a ..... Logic gate. See the figure




- EXOR
- NOT
- NAND

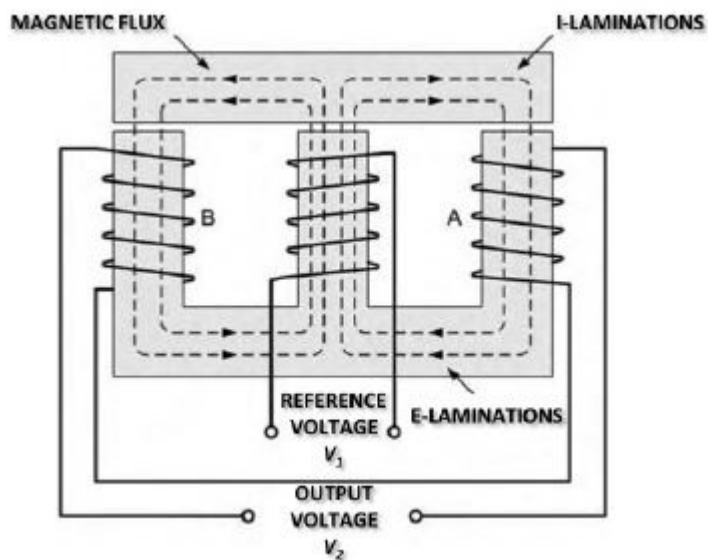30. The two secondary windings of an E&I transformer produce....



- a. out of phase voltages.
- b. in phase voltages.
- c. equal and in phase voltages.

31. This is a diagram of....

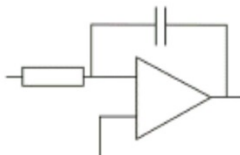

- a. an adder
- b. a differentiator
- c. an integrator

32. The input resistance to an inverting op-amp is 100  $\Omega$ . The feedback resistance is 100 k $\Omega$ . What is the amplifier gain?

- a. 1000
- b. 1/1000
- c. -1000

33. When does an amplifier become unstable and starts to oscillate (i.e. It generates an output without an input being present)?

- a. By applying negative feedback.

- b. By coupling it to a transformer.
- c. By applying positive feedback.

**34.** What is the maximum operating temperature for PCB FR-4 laminate?

- a. 225 °C
- b. 75 °C
- c. 125 °C

**35.** The letters, numbers, symbol and imagery on a circuit board is known as

- a. thieving.
- b. solder mask.
- c. silkscreen.

**36.** A closed loop servomechanism

- a. can have either position or velocity feedback.
- b. must only have position feedback.
- c. must have both position and velocity feedback.

**37.** An open loop system is one which has

- a. position feedback loop.
- b. no direct feedback loop.
- c. rate feedback loop.

**38.** A tachogenerator output is

- a. variable frequency, variable voltage.
- b. variable frequency, constant voltage.
- c. variable voltage, constant frequency.

**39.** The power supply to a synchro system is....

- a. AC or DC
- b. AC
- c. DC

**40.** Reversal of two of the stator connections on a torque synchro receiver would cause

- a. the transmitter to become the receiver.

- b. the output to move in the reverse direction to the input.
- c. the output to move in the same direction as the input.